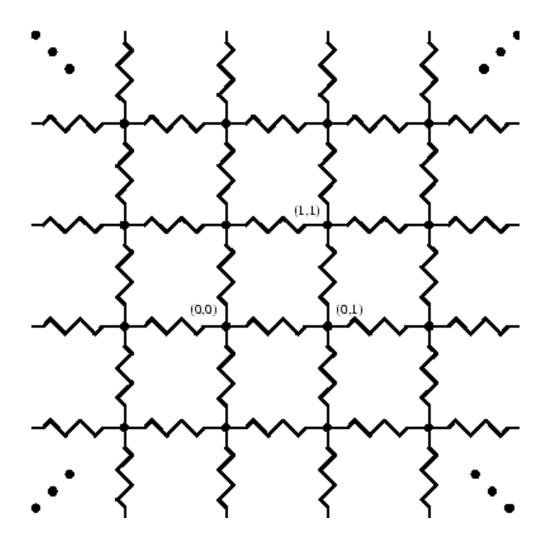
# 11271 Lattice of Resistors

Given an infinite 2D Lattice of resisters as shown below, where the resistance on each edge between neighboring junctions is exactly 1. Pick any junction O and assign the coordinate (0,0). What is the total resistance between O and some other junction J = (i,j)?

**Hint:** There is a surprising Dynamic Programming solution, but how do you get it to fit under the memory requirement? :-) .



### Input

A number of inputs. One test case on each line. The input of each test case is simply the values i, j on a single line. All values will fit inside an unsigned 64 bit integer.

### Output

For each input value, output the total resistance between O and J on a single line. Round to 3 digits after the decimal.

# Sample Input

- 0 0
- 0 1
- 0 2
- 0 3
- 0 4

## **Sample Output**

- 0.000
- 0.500
- 0.727
- 0.861
- 0.954